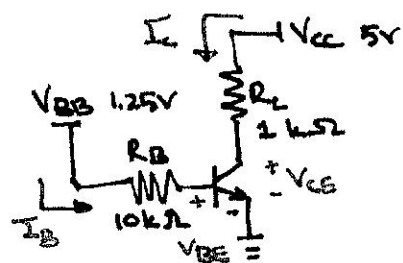


## DEC 2 Refresher



First, check if the BJT is in cutoff:

\*  $V_{BE} \geq 0.7V$ ,  $I_B \geq 0A$   
assumption

$$\therefore \frac{V_{BB} - V_{BE}}{R_B} = I_B = \frac{1.25 - 0.7}{10k} = 55\mu A$$

$\therefore$  not in cutoff.

\*  $\beta \approx 100$   $\rightarrow I_C = \beta I_B = 5.5mA$ .  
assumption

To be in forward active mode,  $V_{CE} \geq 0.2V$ .

$$\therefore V_{CC} - I_C R_C - V_{CE} = 0 \rightarrow V_{CC} - I_C R_C = V_{CE} \rightarrow 5 - 5.5 = V_{CE} = -0.5V.$$

$\therefore$  not in forward active mode; we are in saturation mode.

To push into forward active, let  $V_{CE} = 0.3V$ , backsolve for  $V_{BB}$ .

$$\therefore \frac{V_{CC} - V_{CE}}{R_C} = I_C \rightarrow \frac{4.7}{1000} = 4.7mA \rightarrow I_B = \frac{I_C}{\beta} = 47\mu A.$$

$$\therefore V_{BB} = I_B R_B + V_{BE} = 47 \times 10^{-6} \times 10 \times 10^3 + 0.7 = 1.17V.$$

$\therefore V_{BB}$  can be within the range,  $0.71 < V_{BB} < 1.17 [V]$  to keep in forward active mode.